

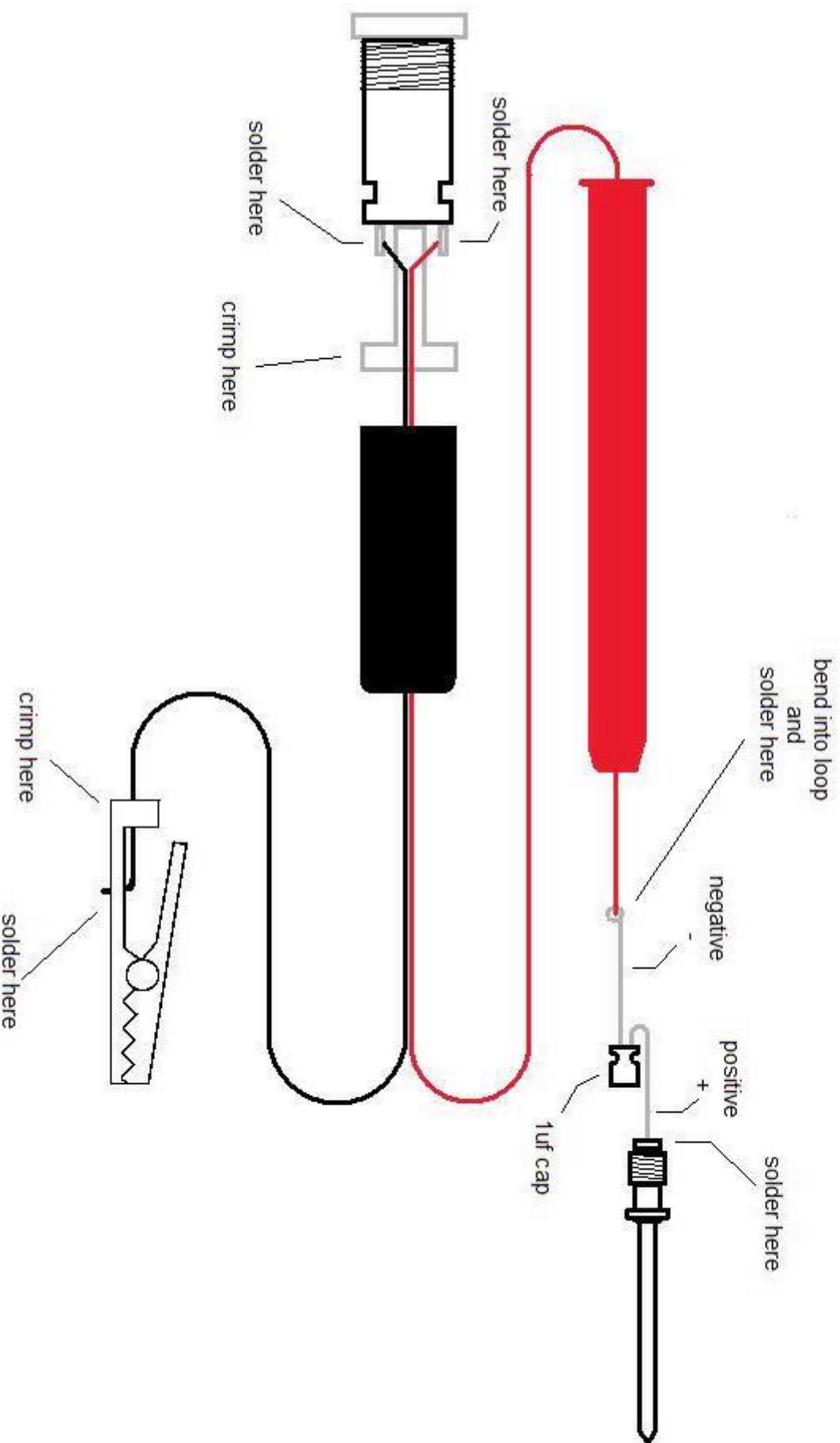


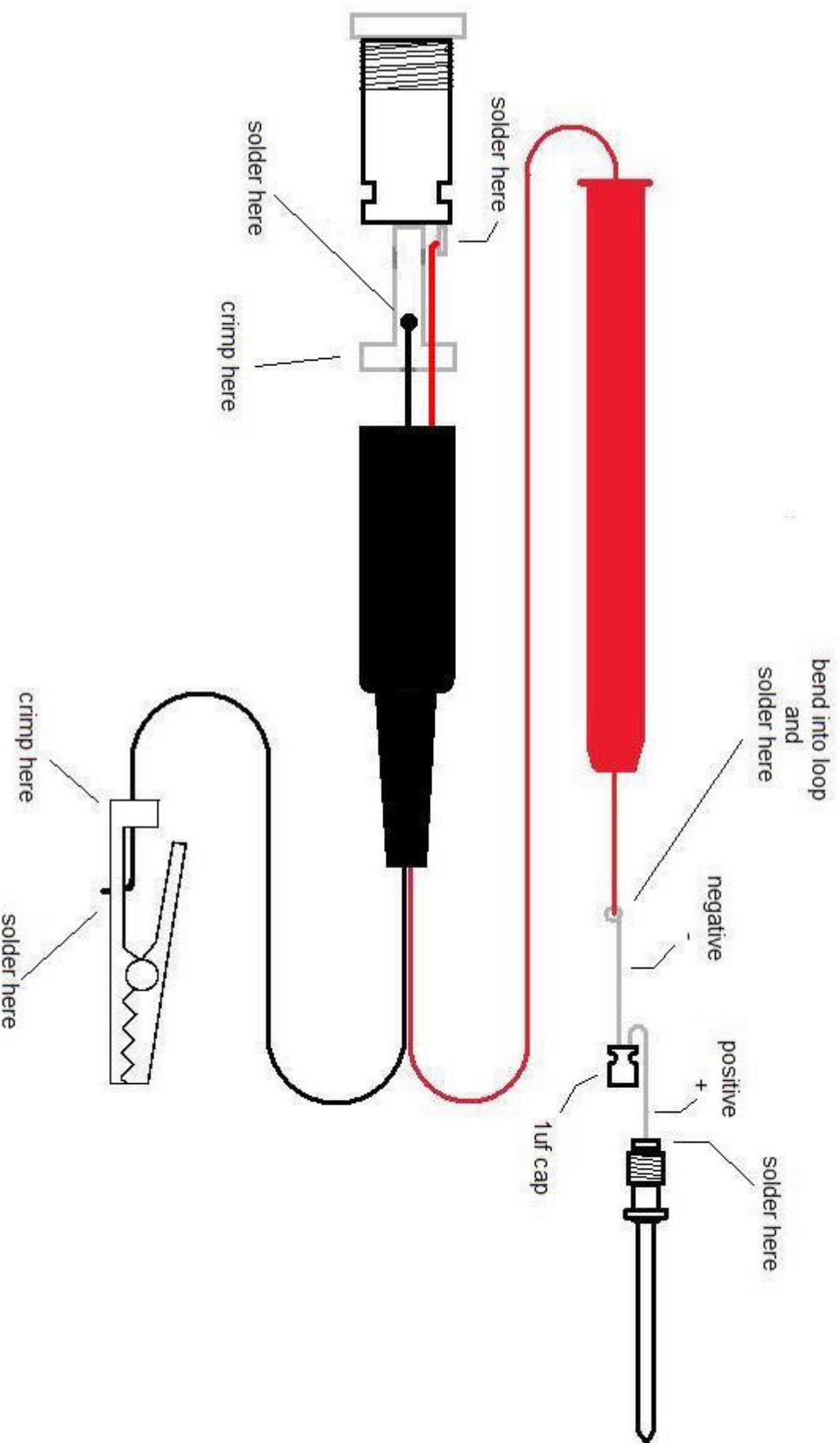Signal Tester Wiring Diagram with stereo jack



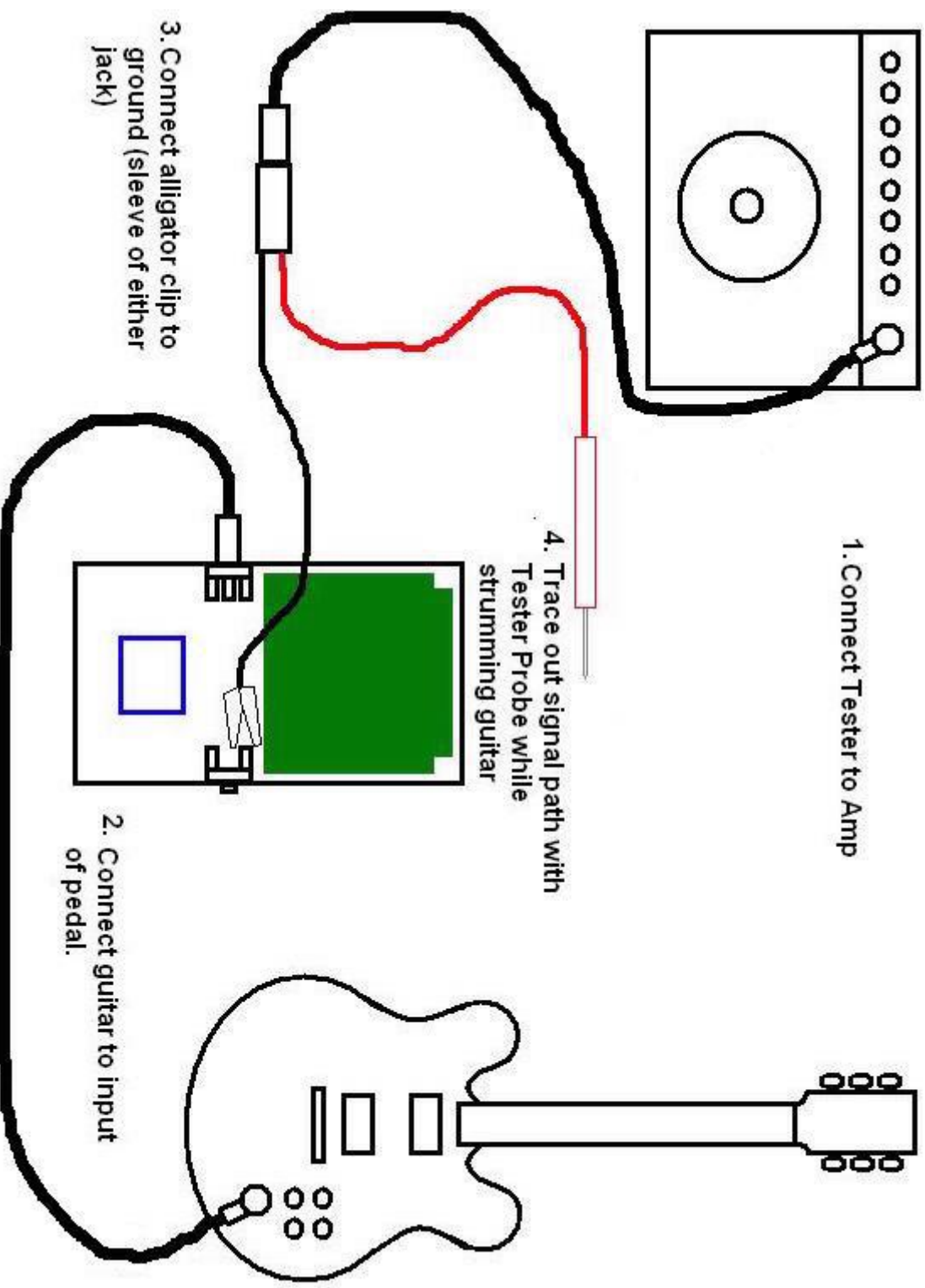Signal Tester Wiring Diagram with mono jack





1. Connect Tester to Amp

4. Trace out signal path with Tester Probe while strumming guitar

2. Connect guitar to input of pedal.

3. Connect alligator clip to ground (sleeve of either jack)